



Experiment No. 3

Title: Design of digital system using Multiplexer.



Batch: B1 Roll No.: 16010420133

Experiment No.: 3

Aim: Design of digital system using Multiplexer..**Resources needed:** Simulation Platform**Theory:**

Multiplexer also called Data selector. A digital circuit which selects one of the 2^n data inputs and route it to the single output. Select lines are (n) and Input lines are (2^n)

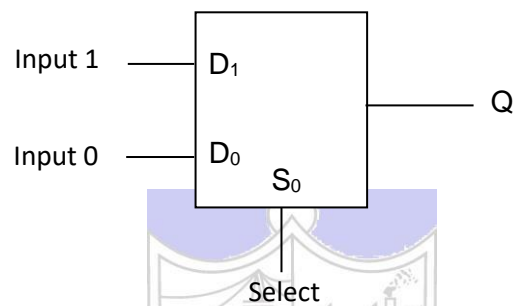


fig 1. A 2 : 1 multiplexer

In this case there are two input terminals D_0 and D_1 , one select input S_0 and one output Q . When the select input is set to logic 0, D_0 is connected to the output. When the select input is set to logic 1, D_1 is connected to the output Q .

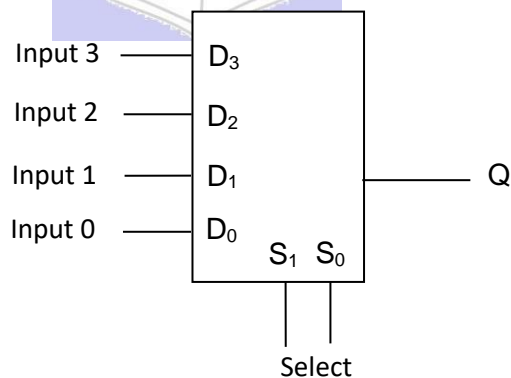


fig 2. A 4 : 1 multiplexer.

In this case there are four data input terminals $D_0 - D_3$, two select inputs S_0 and S_1 and just one output Q . The following truth table shows when each of the data inputs is connected to the output.

Table1. Truth table for 4:1 multiplexer

Select Inputs		Output
S_1	S_0	Q
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

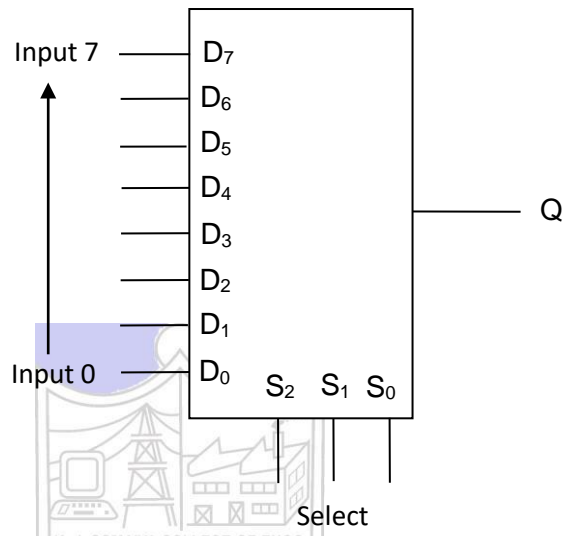


fig 3. An 8 : 1 multiplexer.

Table 2. Truth Table for 8:1 Multiplexer

Select Inputs			Output
S_2	S_1	S_0	Q
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

The above truth table shows when the data inputs are connected to the output.

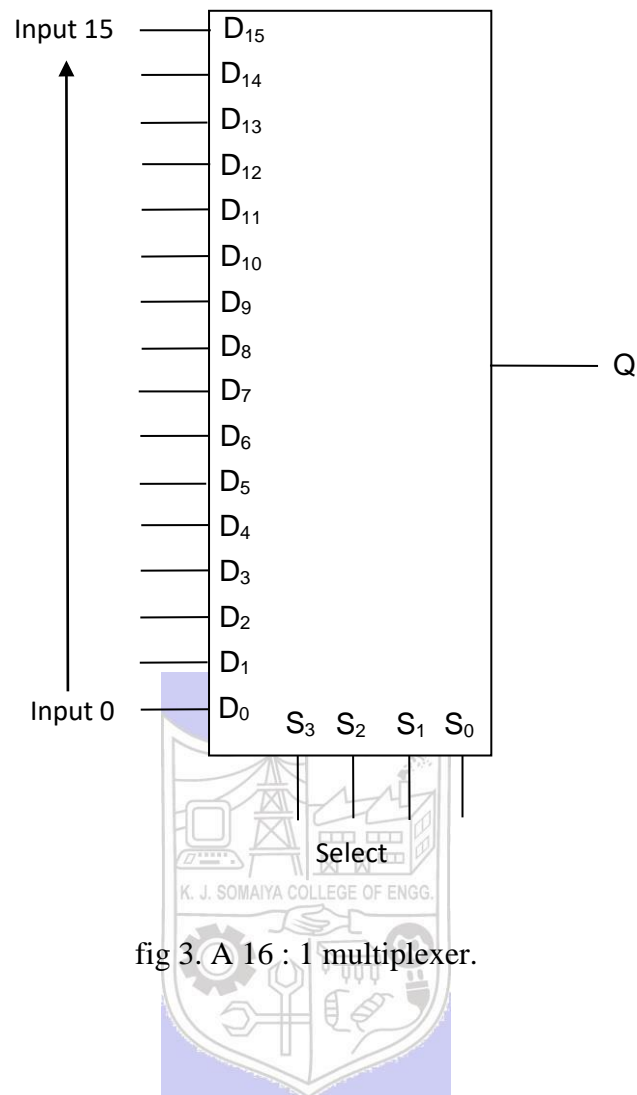


fig 3. A 16 : 1 multiplexer.

The following truth table shows when the data inputs are connected to the output.

Select Inputs				Output
S ₃	S ₂	S ₁	S ₀	Q
0	0	0	0	D ₀
0	0	0	1	D ₁
0	0	1	0	D ₂
0	0	1	1	D ₃
0	1	0	0	D ₄
0	1	0	1	D ₅
0	1	1	0	D ₆
0	1	1	1	D ₇
1	0	0	0	D ₈
1	0	0	1	D ₉
1	0	1	0	D ₁₀
1	0	1	1	D ₁₁
1	1	0	0	D ₁₂
1	1	0	1	D ₁₃
1	1	1	0	D ₁₄
1	1	1	1	D ₁₅

Multiplexers are commonly used in communication systems; however they can be used in Logic System design and simplification as well.



Example 1: Show how a 4 : 1 multiplexer can be used to perform the logic function.

$$f(A,B) = \sum m(0,2,3)$$

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	1
1	1	1

Solution:

CircuitVerse Simulation:

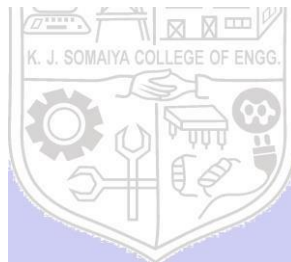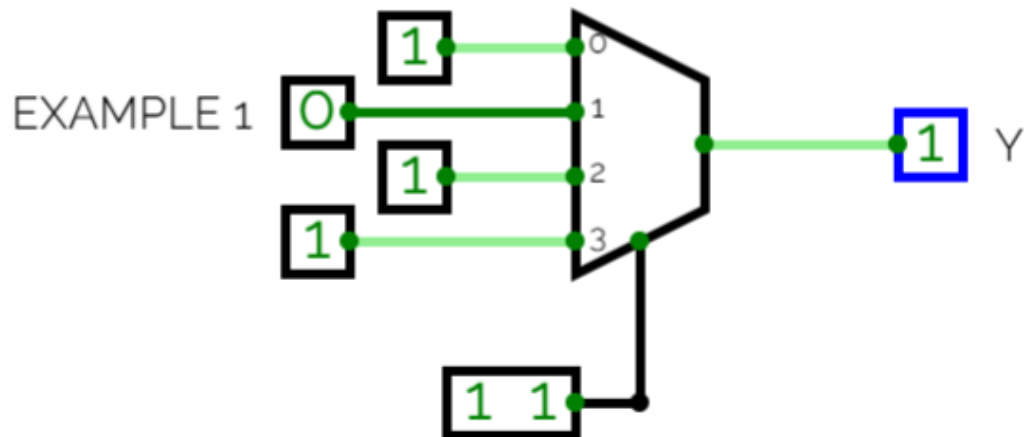



Example 2 : Show how 8 : 1 multiplexer can be used to perform the logic function.(Simulate on circuitverse)

$$F(A,B,C,D) = \sum m(2,3,5,7,10,11,15)$$

Inputs				Output
A	B	C	D	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1


CircuitVerse Simulation:

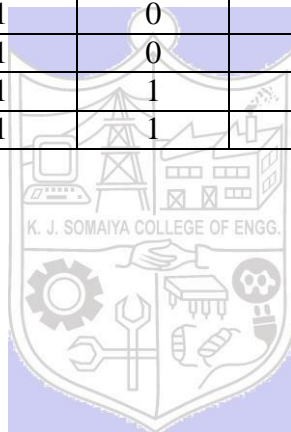

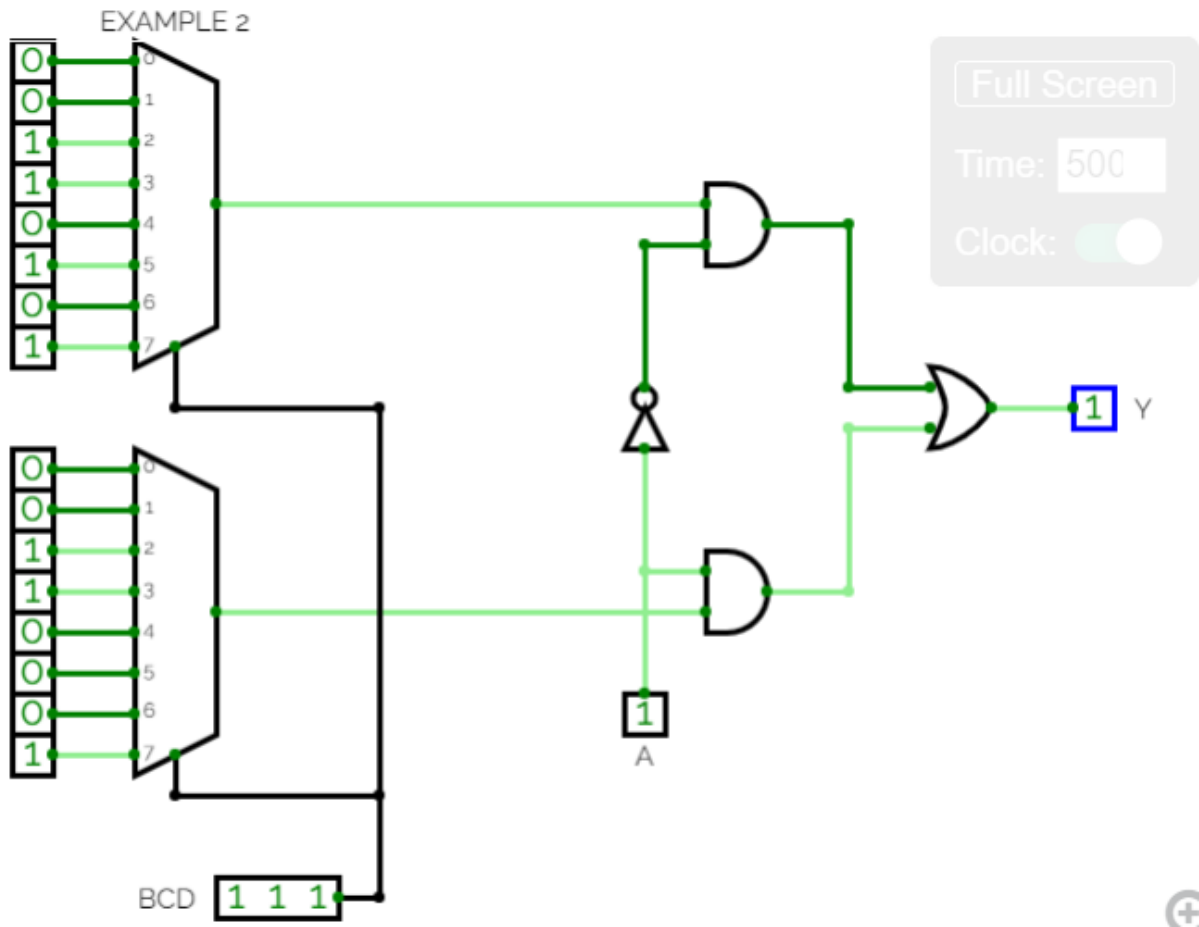

Post lab Question :

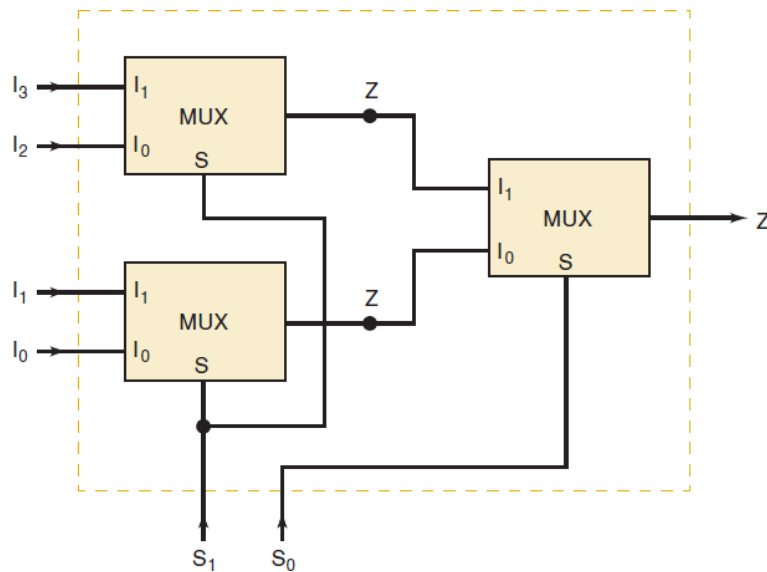a) The circuit in following Figure uses three two-input multiplexers . Determine the function performed by this circuit.



Ans: : $S_1'S_0'I_0 + S_1'S_0I_2 + S_1'S_0'I_1 + S_1S_0I_3$

- The function that the above figure demonstrates is that we can use a three 2-to-1 multiplexers to construct a 4-input multiplexer. It serves as a substitute to the 4-input multiplexer.
- A 4x1 multiplexer has four data inputs I_3, I_2, I_1 & I_0 , two selection lines s_1 & s_0 and one output.

Procedure:

- Design logic circuits for given examples.
- Simulate the circuit for example 2 and verify the outputs.
- Upload the write-up with the solved design problems given in write-up.

Observations and Results: Solve the examples as given in write-up/given during Lab session and simulate as per instructions in Lab session

Outcomes: Design the combinational and sequential circuits using basic building blocks

Conclusion:

From the above experiment we can conclude that we successfully designed and verified the implementation of the circuit by using a multiplexer.

Grade: AA / AB / BB / BC / CC / CD /DD

Signature of faculty in-charge with date

References:

Books/ Journals/ Websites:

1. R. P. Jain, “Modern Digital Electronics”, Tata McGraw Hill.
2. <http://www.scribd.com/doc/78927750/16-1-Mux-Using-8-1-Mux-4-1mux-And-2-1-Mux#scribd>
3. <http://he-coep.virtual-labs.ac.in>

