



**Experiment No. 2**

**Title: Design combinational logic circuit using Logic Gates.**



**Batch: B1****Roll No.: 16010420133****Experiment No.: 2****Aim:** Design combinational logic circuit using Logic Gates.**Resources needed:** Simulation Platform**Theory:**

What is Combinational Logic Circuit?

Ans:

Combinational circuit is a circuit in which we combine the different gates in the circuit, for example encoder, decoder, multiplexer and demultiplexer. Some of the characteristics of combinational circuits are following –

- The output of combinational circuit at any instant of time, depends only on the levels present at input terminals.
- The combinational circuit do not use any memory. The previous state of input does not have any effect on the present state of the circuit.
- A combinational circuit can have an n number of inputs and m number of outputs.

**Block diagram****Procedure:**

- Design combinational circuit for
  - 4 bit Binary to Gray code converter
  - 4 bit Even Parity checker
- Simulate both the designed circuits.
- Verify the designed truth table.
- Upload the Schematic Diagram generated on Simulation Software as well as Writeup containing Questions asked in writeup, CO and Conclusion.
- Please note every document uploaded on google classroom should be labelled as Exp\_<No>\_<RollNo>\_<schematic/writeup>.pdf

**Observations and Results: Observe the output for different input combinations.**

**Problem:** To design 4 bit Binary to Gray code converter

**Outcomes:-**

**Inputs:**  $B_3B_2B_1B_0$

**Outputs:**  $G_3G_2G_1G_0$

Input				Output			
B3	B2	B1	B0	G3	G2	G1	G0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0


**Expressions are:-**

$$G_3=B_3$$

$$G_2=B_3 \oplus B_2$$

$$G_1=B_2 \oplus B_1$$

$$G_0=B_1 \oplus B_0$$

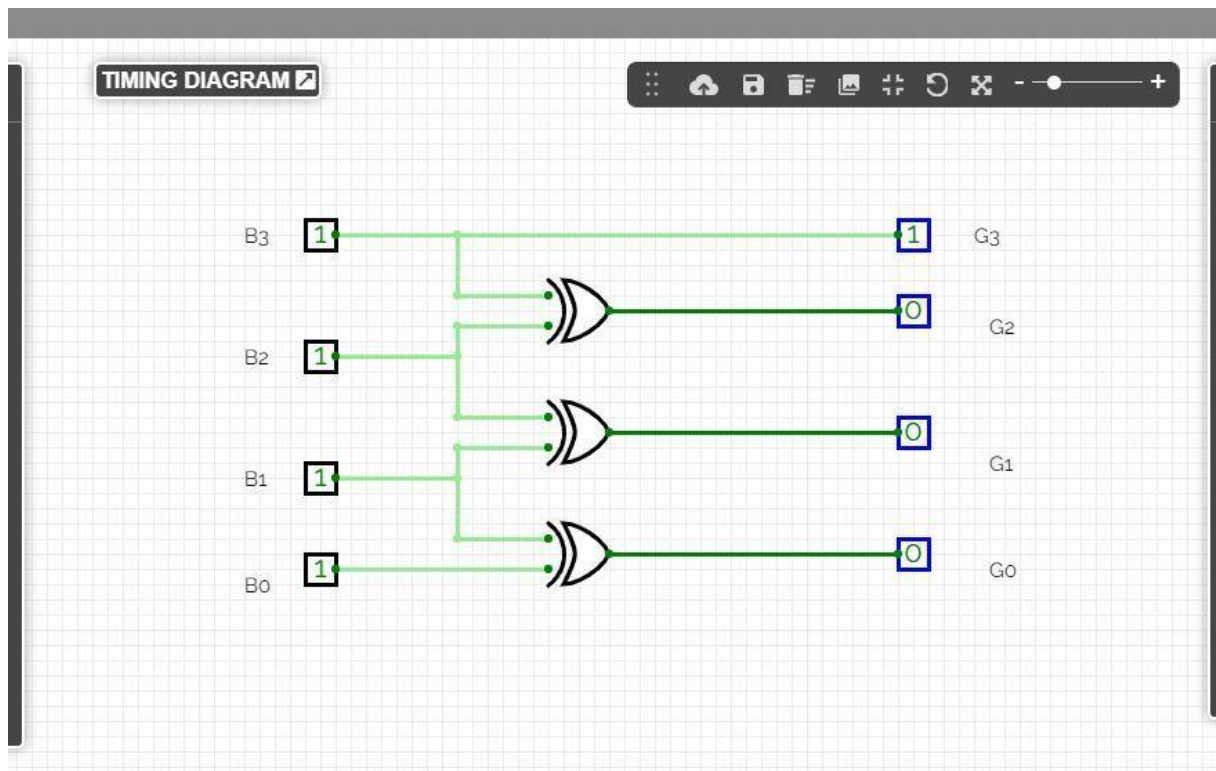**Simulation:-**

**Problem:** To design a 4 bit Even Parity Checker

**Inputs:** ABCD


**Output:** Y

**Truth Table:**

Considering,  
0 to be No error  
1 to be error

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

**CircuitVerse Simulation:**

 

---

**Outcomes:** Design the combinational and sequential circuits using basic building blocks

---

**Conclusion:**

**In this chapter, the design of basic cells has been reviewed. The specific design of the XOR gate has been detailed, as well as the complex gates.**

**Grade: AA / AB / BB / BC / CC / CD /DD**

**Signature of faculty in-charge with date**

---

**References:**

**Books/ Journals/ Websites:**

R. P. Jain, “Modern Digital Electronics”, Tata McGraw Hill

